



EE 2210 – Circuits and Fields

Assignment: Passive Filter Design

Index No : 230675D

Name : Vithanage S.V.C.H.

1.

230675D

Circuits and Fields Assignment

① Woofer low pass = (-12 dB/oct) -
 Tweeter high pass = (-12 dB/oct)
 Midrange band pass = (24 dB/oct)

As Butterworth has 6 dB/oct or 20 dB/dec ;

Woofer \rightarrow 2nd order $(12/6 = 2)$
 Tweeter \rightarrow 2nd order $(12/6 = 2)$
 Midrange \rightarrow 8th order $(24/6 = 4 + 4 = 8)$

② $\Delta \text{dB} = \text{slope} \times \log_2 \left(\frac{f}{f_0} \right)$ (as 2x of 'f' shows ΔdB differe.)

\therefore for woofer;

$$-3 - (-6) = (-12) \times \log_2 \left(\frac{f}{100} \right)$$

$$f_c = 84.09 \text{ Hz} \approx \boxed{84 \text{ Hz}}$$

\therefore at woofer $-3 \text{ dB} \rightarrow \boxed{84 \text{ Hz} = f_c}$

for tweeter;

$$-3 - (-6) = 12 \times \log_2 \left(\frac{f_c}{2000} \right)$$

$$f_c = 2378.4 \text{ Hz}$$

at tweeter, $-3 \text{ dB } f_c \rightarrow \boxed{2378 \text{ Hz}}$

at Midrange;

$$f_{c1} = 2^{-1/8} \times 100 = \boxed{109 \text{ Hz}}$$

$$f_{c2} = 2^{+1/8} \times 2000 = \boxed{1834 \text{ Hz}}$$

(The roll-off rate is determined by the filter's order, n , and is expressed as $20n$ dB per decade or $6n$ dB per octave)

2. Therefore, from the above plot and calculations;

Woofer (Low Pass Filter) Cut off frequency : 84 Hz

Tweeter (High Pass Filter) Cut off frequency : 2378 Hz

Midrange (Band Pass Filter) Cut off frequency : 109 – 1834 Hz

3. Filter Calculations:

③ Pass band tolerance = 3dB
Attenuation = -90dB @ $f = 5f_c$

$$\therefore 10 \lg(1 + \epsilon^2) = 3 \quad \text{and} \quad 10 \lg\left(1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}\right) = 90$$

$$\boxed{\epsilon \approx 1}$$

$$1 + \epsilon^2 (5)^{2N} = 10^9$$

$$\boxed{N = 7^{\text{th}} \text{ order}} \quad \leftarrow \quad \therefore N = 6.438$$

\therefore Transfer funct. $|H(\omega)|^2 = \frac{k}{1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}}$; $S = j\left(\frac{\omega}{\omega_c}\right)$

Normalized butterworth for low pass

Normalized circuit - low pass - order 7 :-

Denormalizing:

$$L \rightarrow \left[L = \frac{L_n R_o}{\omega_c} \right] \quad ; \quad R_o = 50 \Omega \quad \omega_c = 2\pi \times 84$$

$$C \rightarrow \left[C = \frac{C_n}{\omega_c \times R_o} \right]$$

$R_1 = 50 \Omega //$

$L_1 = \frac{0.445 \times 50}{2\pi \times 84} = 42.16 \text{ mH} //$

$C_2 = \frac{1.247}{2\pi \times 84 \times 50} = 47.95 \mu\text{F} //$

$L_3 = \frac{1.8019 \times 50}{2\pi \times 84} = 170.7 \text{ mH} //$

$C_4 = \frac{2}{2\pi \times 84 \times 50} = 75.78 \mu\text{F} //$

$L_5 = \frac{1.8019 \times 50}{2\pi \times 84} = 170.7 \text{ mH} //$

$C_6 = \frac{1.247}{2\pi \times 84 \times 50} = 47.25 \mu\text{F} //$

$L_7 = \frac{0.445 \times 50}{2\pi \times 84} = 42.16 \text{ mH} //$

$R_2 = 50 \Omega //$

high pass transfer function:

$$|H(j\omega)|^2 = \frac{K}{1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}} \quad ; \quad s = j\left(\frac{\omega}{\omega_c}\right)$$

$$= \frac{s^7}{s^7 + 4.494\omega^2 s^6 + 10.698\omega^2 s^5 + \dots}$$

($\omega = 22 \times 2378$)

Transfer function of Band Pass

$$H(s) = \frac{1 + Y(s)}{1 - Y(s)} \rightarrow Y(s) = \frac{s^7}{s^7 + 4.494\omega^2 s^6 + 10.698\omega^2 s^5 + \dots}$$

$$H(s) = H_L \times H_H$$

$$= \left[\frac{K}{1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}} \right] \left[\frac{K}{1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}} \right] \quad \omega =$$

$$= \frac{\omega_1^7}{(s^7 + 4.494\omega^2 s^6 + \dots)} \times \left(\frac{s^7}{s^7 + 4.494\omega^2 s^6 + \dots} \right)$$

Transfer Functions for low pass filter and high pass filter:

Low pass transfer:

$$|H(j\omega)|^2 = \frac{K}{1 + \epsilon^2 \left(\frac{\omega}{\omega_c}\right)^{2N}} \quad ; \quad s = j\left(\frac{\omega}{\omega_c}\right)$$

$$= \frac{1}{1 + \left(\frac{s}{j}\right)^{2 \times 7}} = \frac{1}{1 - s^{14}}$$

$$Y(s) Y(s) = 1 - \frac{(R_L R_i) |H(s)|^2}{(R_H R_L)^2}$$

$$= 1 - \frac{1}{1 - s^{14}} = \frac{-s^{14}}{1 - s^{14}} \quad ; \quad (-s^7)(1 + s^7)$$

$$Y(s) Y(s) = \frac{s^7 - s^7}{(1 + s^7)(1 - s^7)}$$

$$Y(s) = \frac{s^7}{1 + s^7}$$


$$Z(s) = \frac{1 + Y(s)}{1 - Y(s)} = \frac{1 + 2s^7}{1 - s^{14}}$$

for high pass:

$$= \frac{K}{1 + \epsilon^2 \left(\frac{j}{s}\right)^{14}} = \frac{s^{14}}{s^{14} - 1} = \frac{s^7 + s^7}{(s^7 - 1)(s^7 + 1)}$$


$$Y(s) Y(s) = \frac{-1}{s^{14} - 1} \rightarrow Y(s) = \frac{1}{s^7 + 1} \quad ; \quad Z(s) = \frac{1 + Y(s)}{1 - Y(s)}$$

∴ Low Pass filter circuit

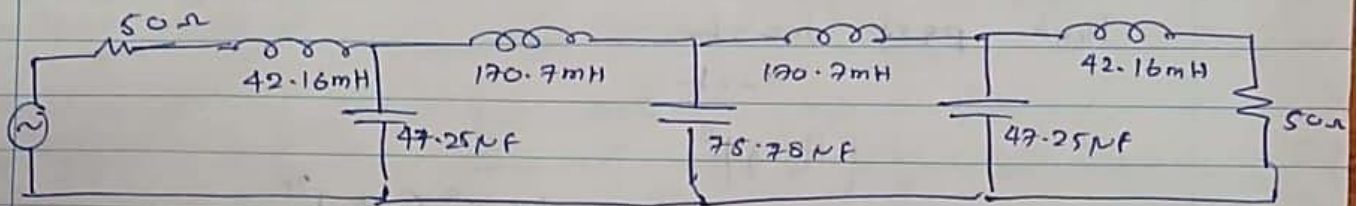

High Pass Normalized Circuit

$$\omega = 2\pi \times 2378$$

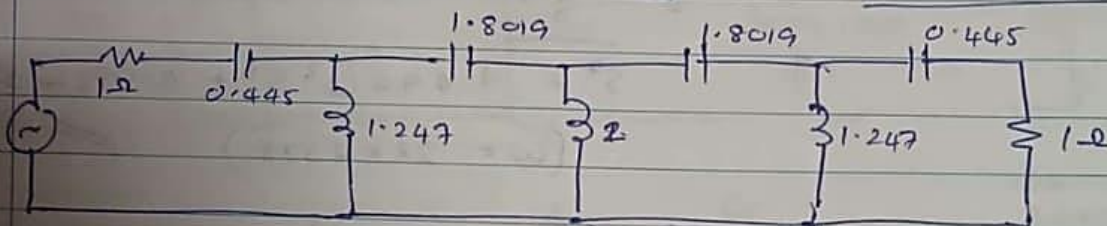

Denormalizing

$$L \rightarrow \frac{1}{\omega L R}$$

$$C \rightarrow \frac{R}{\omega C}$$

$$R_1 = 50 \Omega$$

$$C_1 = \frac{1}{2\pi \times 2378 \times 0.445 \times 50} = 3 \mu F //$$

$$L_4 = \frac{50}{2\pi \times 2378 \times 2} = 1.67 \text{ mH} //$$

$$L_2 = \frac{50}{2\pi \times 2378 \times 1.247} = 2.68 \text{ mH} //$$

$$C_5 = \frac{1}{2\pi \times 2378 \times 1.8019 \times 50} = 0.74 \mu F //$$


$$C_3 = \frac{1}{2\pi \times 2378 \times 1.8019 \times 50} = 0.74 \mu F //$$

$$L_6 = \frac{50}{2\pi \times 2378 \times 1.247} = 2.68 \text{ mH} //$$

$$C_7 = \frac{1}{2\pi \times 2378 \times 0.445 \times 50} = 3 \mu F //$$

$$R_2 = 50 \Omega //$$

high pass filter circuit

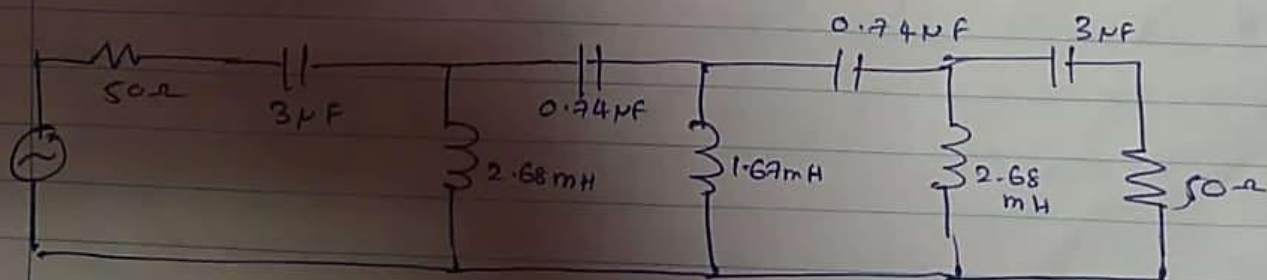

Band Pass Filter

$$R_1 = R_2 = 50 \Omega$$


$$f_1 = 109 \text{ kHz} \rightarrow \omega_{c1} = 684.867 \text{ rad/s}$$

$$f_2 = 1834 \text{ kHz} \quad \omega_{c2} = 11523.36 \text{ rad/s}$$


$$\text{BW} = \omega_{c2} - \omega_{c1} = 10838.5 \text{ rad/s}$$

$$\omega_0 = \sqrt{\omega_{c1} \times \omega_{c2}} = 2809.27 //$$

Normalized Low P

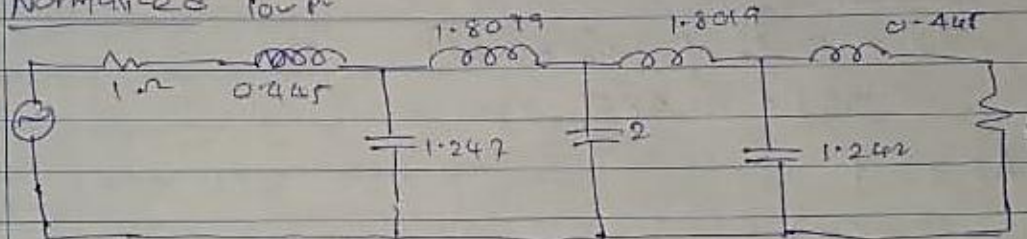

Apply for band pass

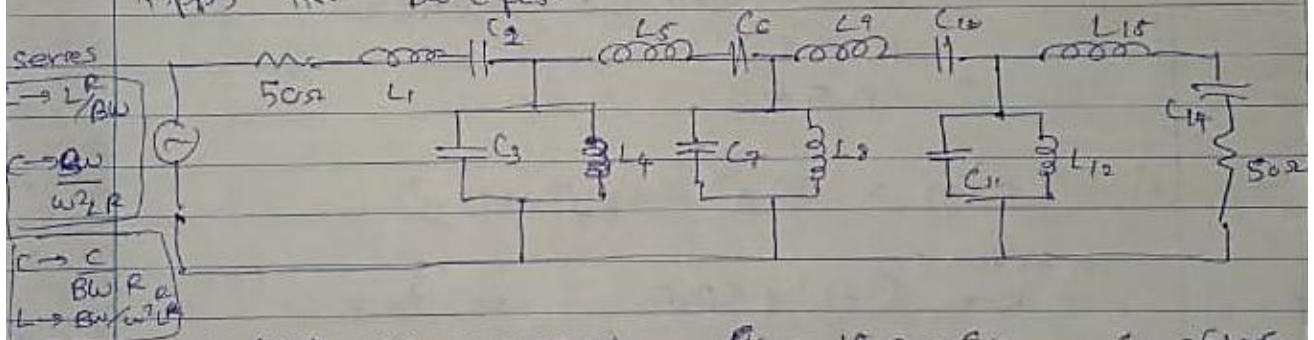

$$L_1 = \frac{0.445 \times 50}{10838.5} = 2.05 \text{ mH} // \quad C_2 = 15.2 \text{ pF} // \quad C_{14} = 61 \text{ pF} //$$

$$C_2 = \frac{10838.5}{(2809.27)^2 \times 0.445 \times 50} = 61 \text{ pF} // \quad L_7 = 3.7 \text{ uF} //$$

$$C_3 = \frac{1.242}{10838.5 \times 50} = 2.29 \text{ pF} //$$

$$L_8 = 34.2 \text{ mH} //$$

$$L_9 = 8.31 \text{ mH} //$$

$$L_4 = \frac{10838.5 \times 50}{(2809.27)^2 \times 1.242} = 53 \text{ mH} //$$

$$C_{10} = 15.2 \text{ pF} //$$


$$C_{11} = 2.29 \text{ pF} //$$

$$L_5 = \frac{1.8019 \times 50}{10838.5} = 8.31 \text{ mH} //$$


$$L_{12} = 53 \text{ mH} //$$

$$L_{15} = 2.05 \text{ mH}$$


➤ LTspice Schematic: Low Pass Filter

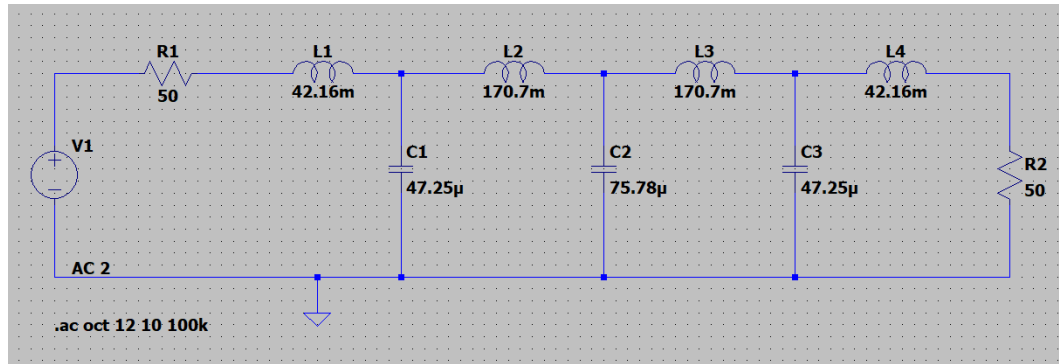


➤ LTspice Simulation:

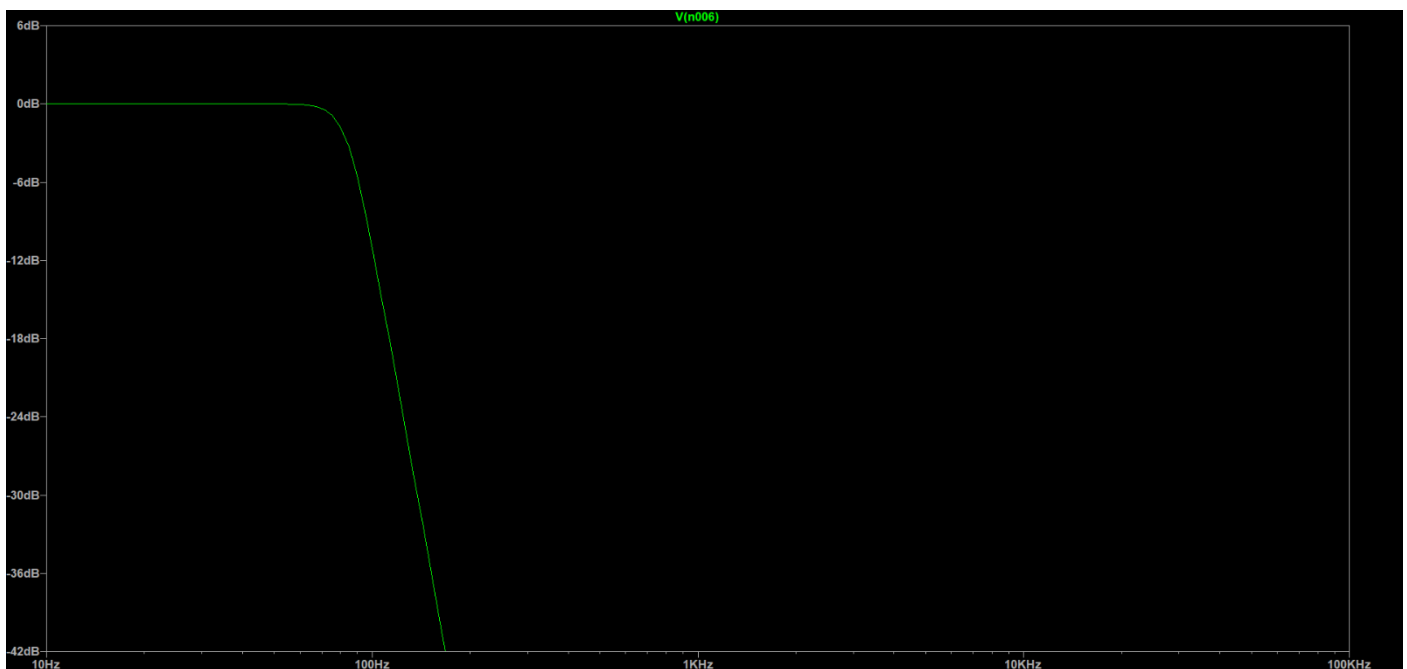

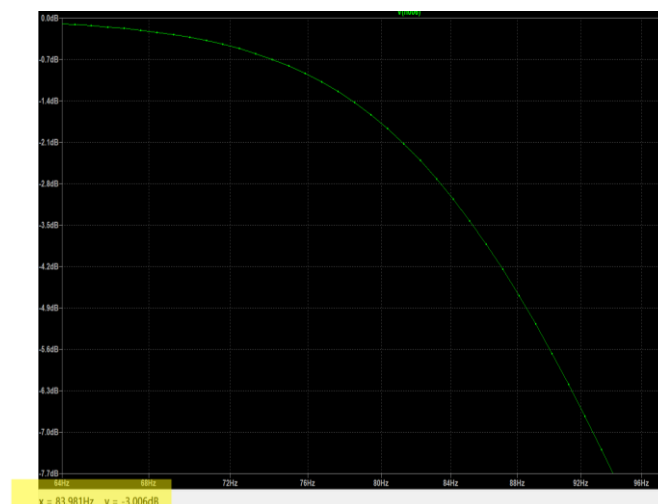
From this Cut off frequency (-3 dB) is 84 Hz.




➤ LTspice schematic: High Pass Filter

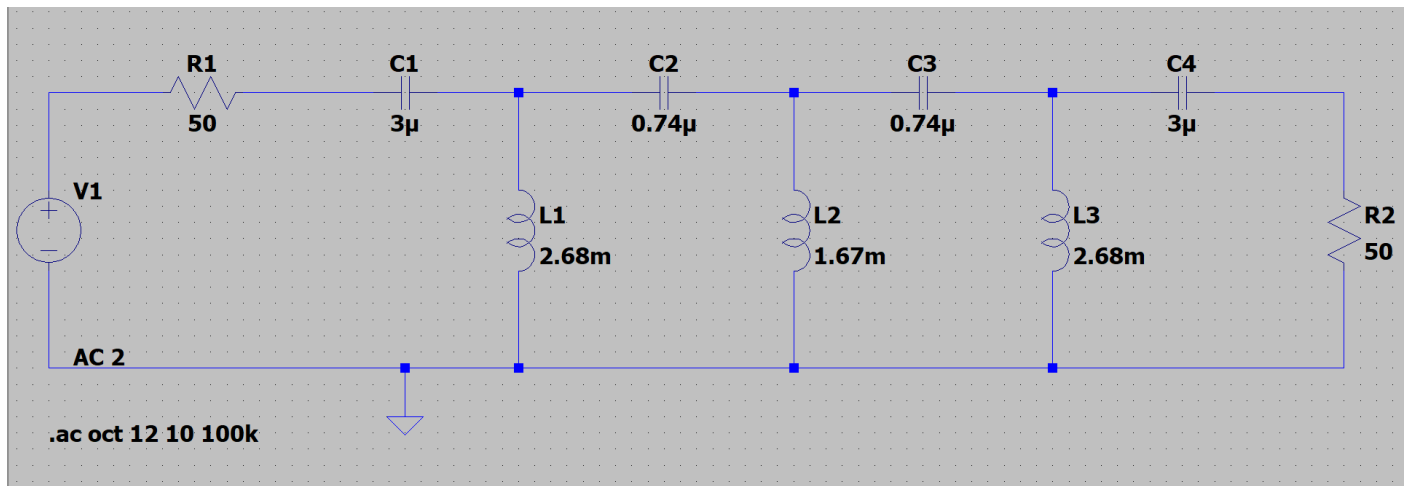


➤ LTspice simulation: High Pass Filter

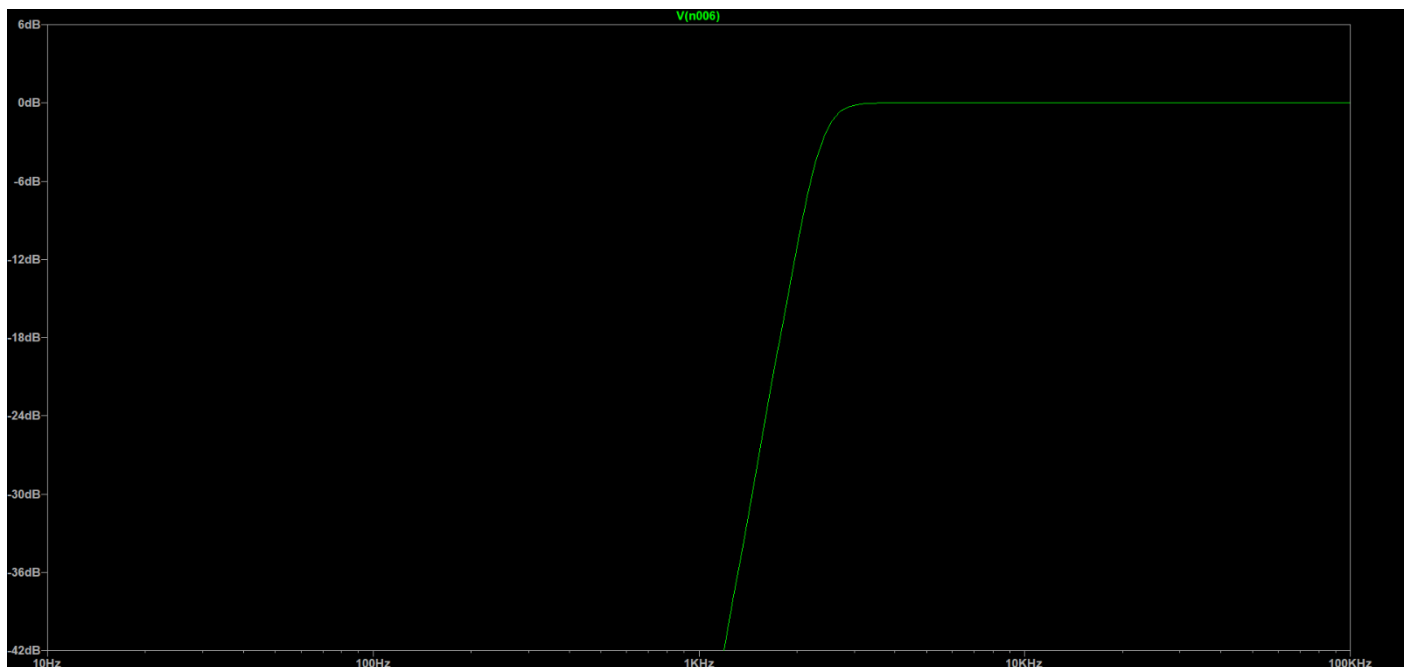

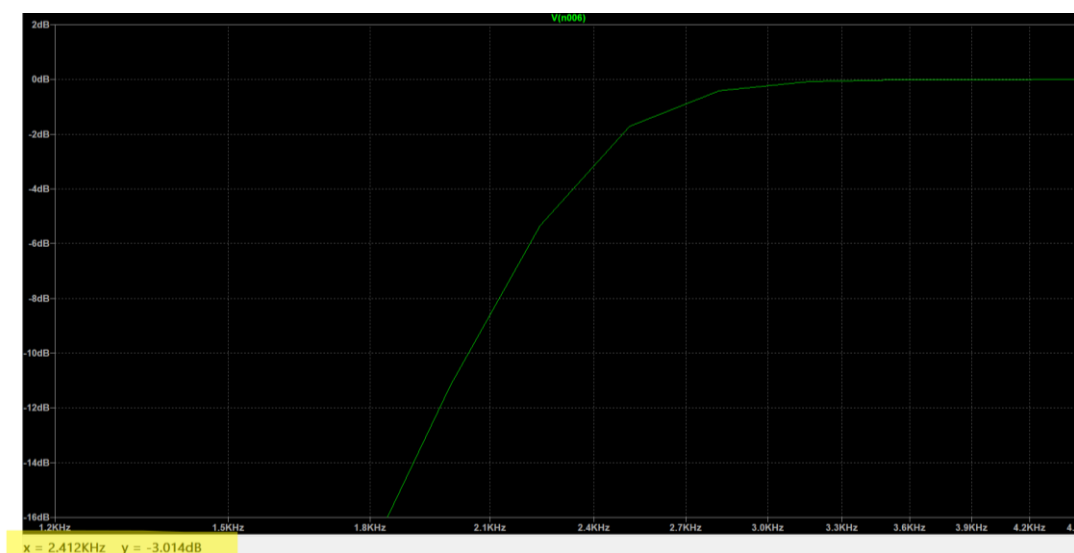
From this plot Cut off frequency is 2412 Hz.



➤ LTspice schematics: Band Pass Filter


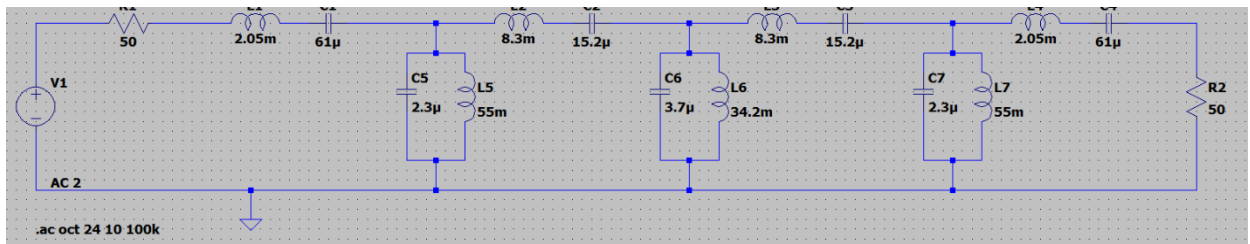


➤ LTspice Simulation:

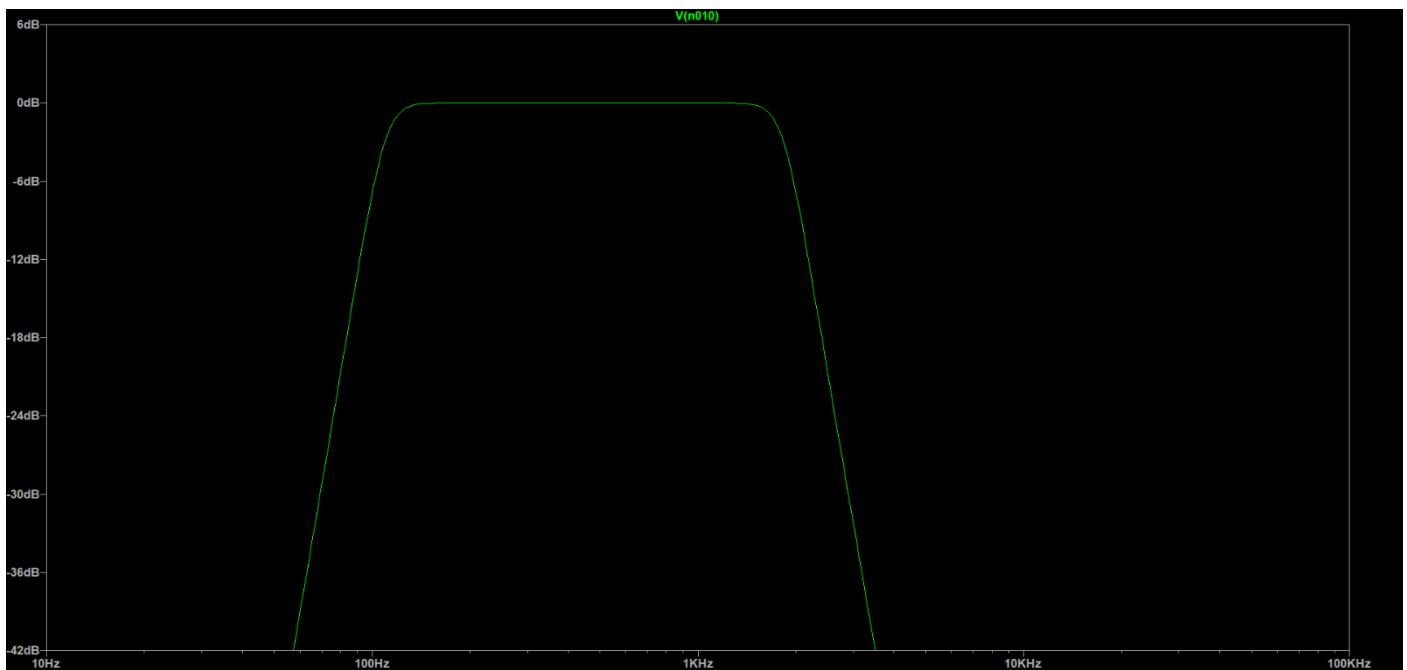

From this Pass Band frequencies are 109.3 Hz – 1832 Hz.

➤ Comparison:

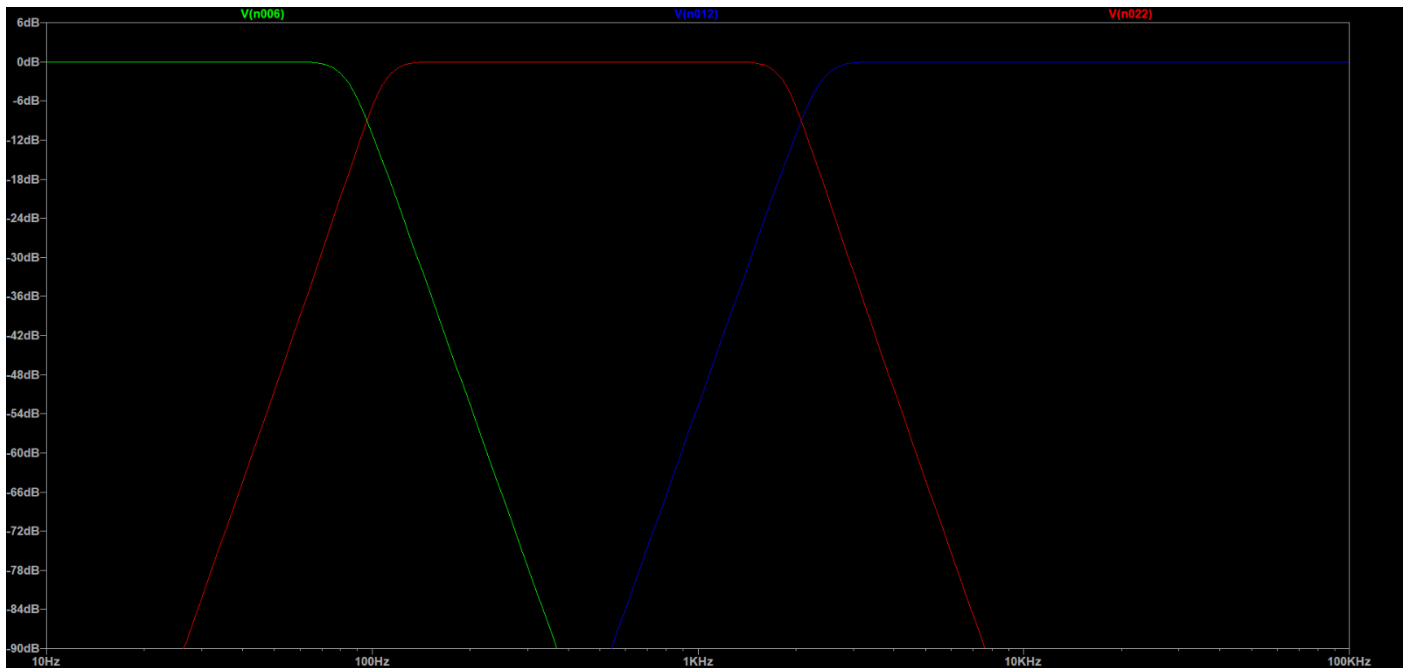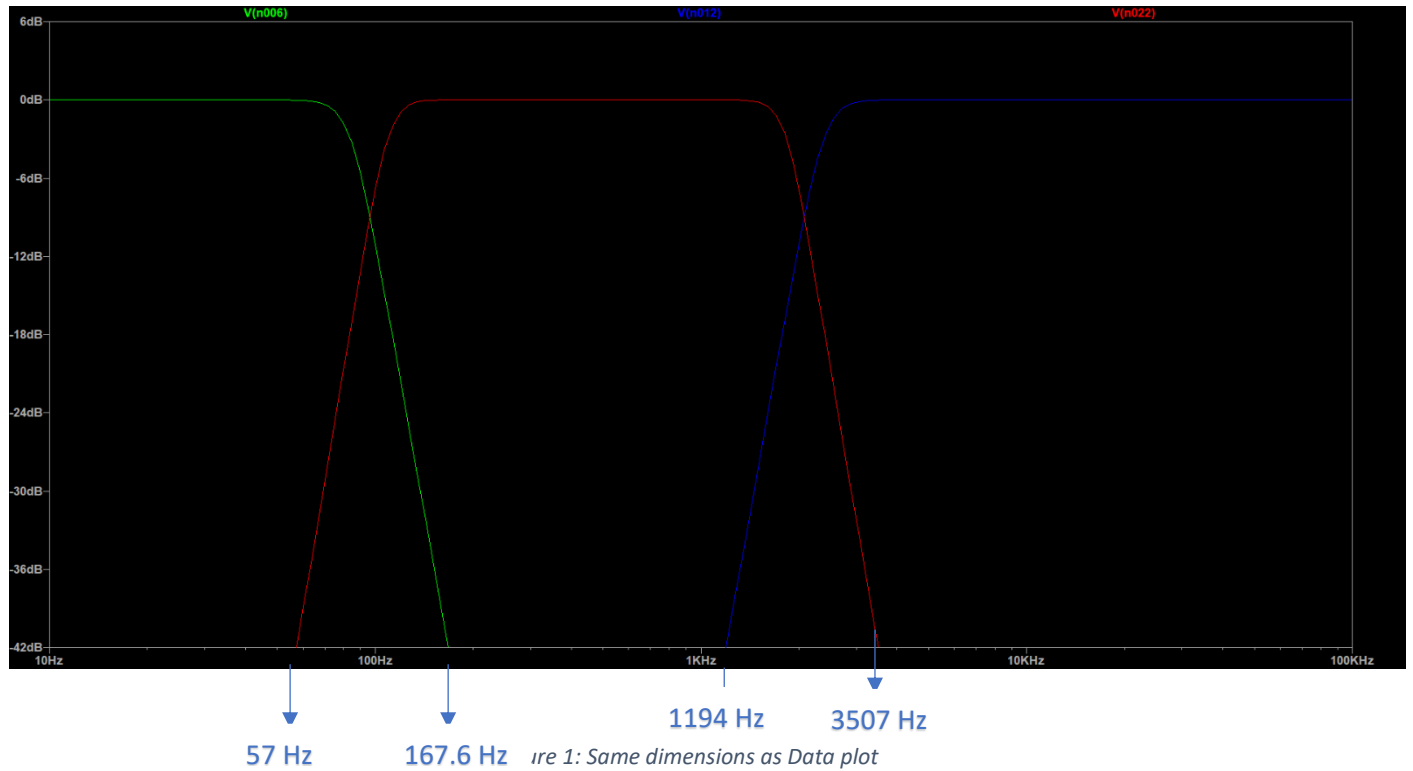

In data plot the cross-over frequency of woofer and midranger is 100 Hz , -6 dB. The LTspice simulation gives cross over frequency of 96 Hz, -9dB.

In data plot upper cross over frequency is 2000 Hz, -6dB. LTspice simulation gives cross over frequency of 2078 Hz , -9 dB.

In transition band of woofer and midranger(Low end and low pass band of woofer):

the frequency difference from plot : $167 - 57 = 110 \text{ Hz}$

Data plot value for the transitional band : $300 - 20 = 280 \text{ Hz}$

Therefore, reduction in region : $280 - 110 = 170 \text{ Hz}$

In transition band of midranger and Tweeter. (High end and high pass filter)

frequency difference : $3507 - 1194 = 2313 \text{ Hz}$

Data plot value for the transitional band : $7000 - 600 = 6300 \text{ Hz}$

Therefore, reduction in region : $6300 - 2313 = 3987 \text{ Hz}$

4.

Chebyshev type I

$$\text{Passband} = 0.5 \text{ dB}$$

$$\text{Attenuation} = 90 \text{ dB} \quad @ \quad f_c = f$$

$$\therefore y = 5$$

$$0.5 = 10 \lg(1 + \epsilon^2) \rightarrow \epsilon = 0.35$$

$$1 + \epsilon^2 \text{Th}^2(y)$$

$$90 = 10 \lg(1 + \epsilon^2 \text{Th}^2(y))$$

$$\therefore \text{Th}(y) = 9.287$$

As $y > 1$:

$$\text{Th}(y) = \cosh(n \times \cosh^{-1} y)$$

$$9.287 = \cosh(n \times \cosh^{-1} 5)$$

$$n = 5.3$$

$$n \approx 6$$

$$\therefore T_6(y) = 32y^6 - 48y^4 + 18y^2 - 1$$

n - even:


$$k = \frac{(1 + \epsilon^2) 4R_1 R_2}{(R_1 + R_2)^2} = k =$$

$$k = (1 + 0.35^2) \times 1 = 1.1225$$

$$\therefore \text{Trans. for } A_{\text{mag}} = \frac{1.1225}{1 + \epsilon^2 \text{Th}^2(y)}$$

$$= \frac{1.1225}{1 + 0.35^2 (32y^6 - 48y^4 + 18y^2 - 1)}$$

Normalized

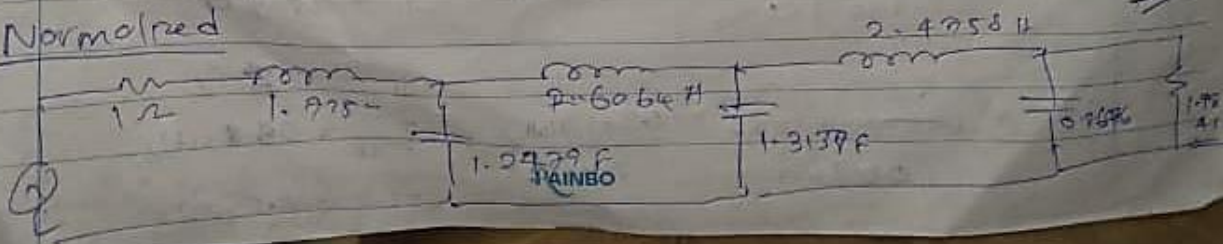

Transfer function remaining part:

$$Y(s)/X(s) = 1 - \frac{4R_1 R_2}{(R_1 + R_2)^2} H(s)^2$$

$$= 1 - 1 \times \left(\frac{1.1225}{(1 + 0.35^2) \left[92 \left(\frac{s}{j} \right)^4 - 43 \left(\frac{s}{j} \right)^2 + 18 \left(\frac{s}{j} \right)^0 \right]} \right)^2$$

Cherbyshev filter De normalizing:

De normalizing for passband tol = 0.5dB

$\omega = 84 \text{ Hz}$

$L_1 = \frac{1.7254 \times 50}{2\pi \times 84} = 163.4 \text{ mH}$

$C_2 = \frac{1.2479}{2\pi \times 84 \times 50} = 47.3 \text{ pF}$

$L_3 = \frac{2.26064 \times 50}{2\pi \times 84} = 246.8 \text{ mH}$

$C_4 = \frac{1.3137}{2\pi \times 84 \times 50} = 49.8 \text{ pF}$


$L_5 = \frac{2.4758 \times 50}{2\pi \times 84} = 234.6 \text{ mH}$

$C_6 = \frac{0.8696}{2\pi \times 84 \times 50} = 33 \text{ pF}$


$R_2 = 99.2 \Omega$

circuit for cheby Type I filter

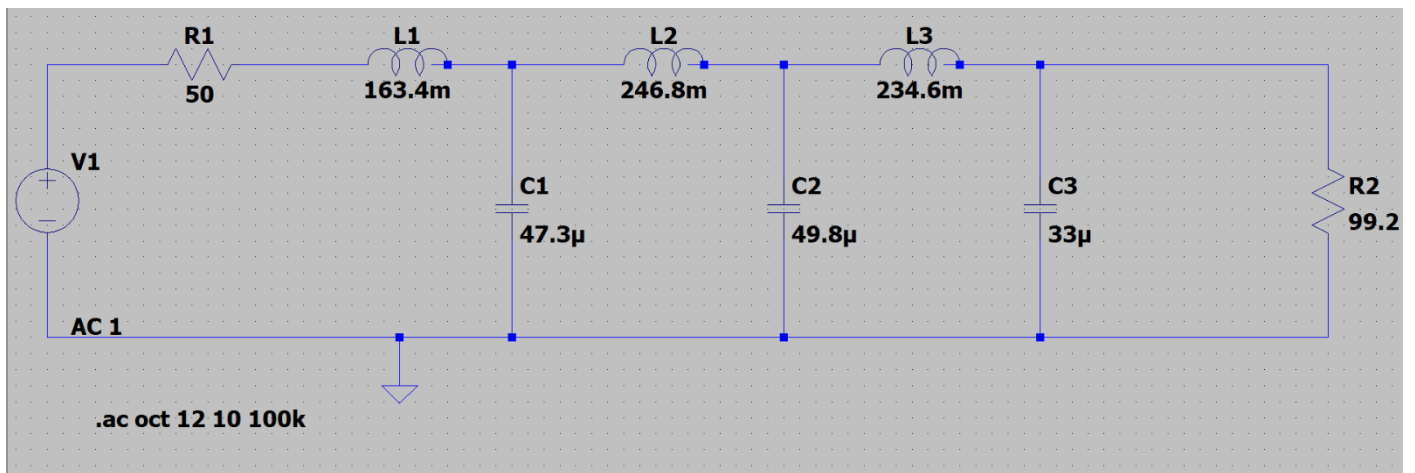
➤ LTspice schematics: Cherbyshev I filter



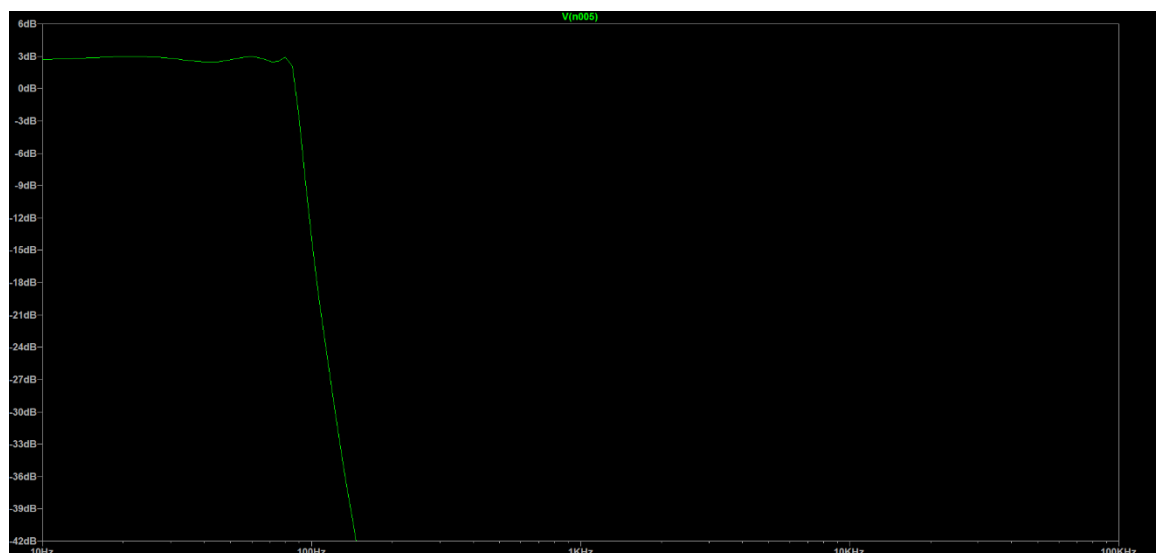
➤ LTspice simulation:
Here using voltage amplitude 2 V.



Here using voltage amplitude 1 V.

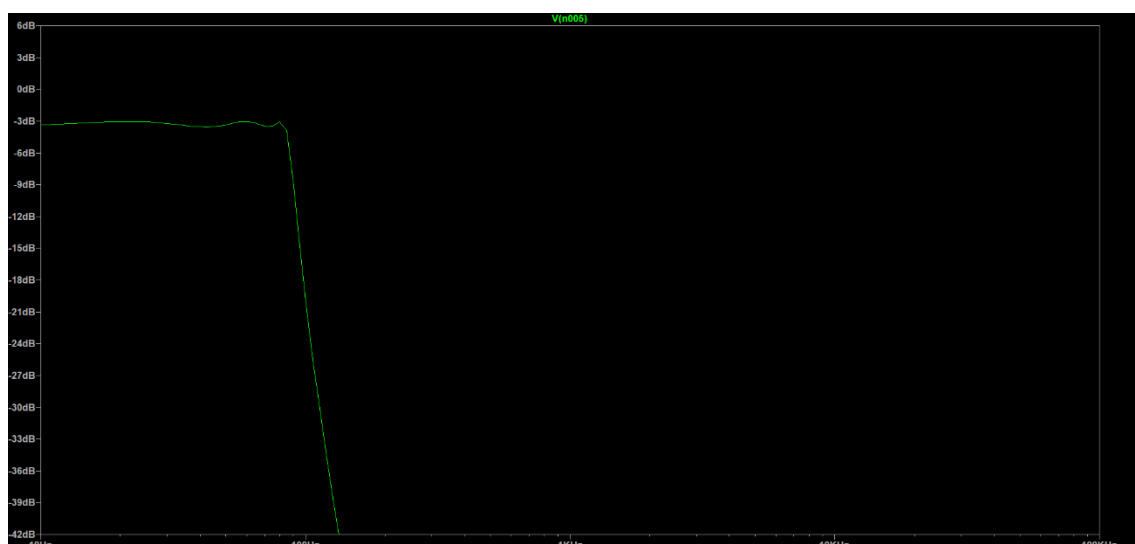

➤ Comparing two filters:

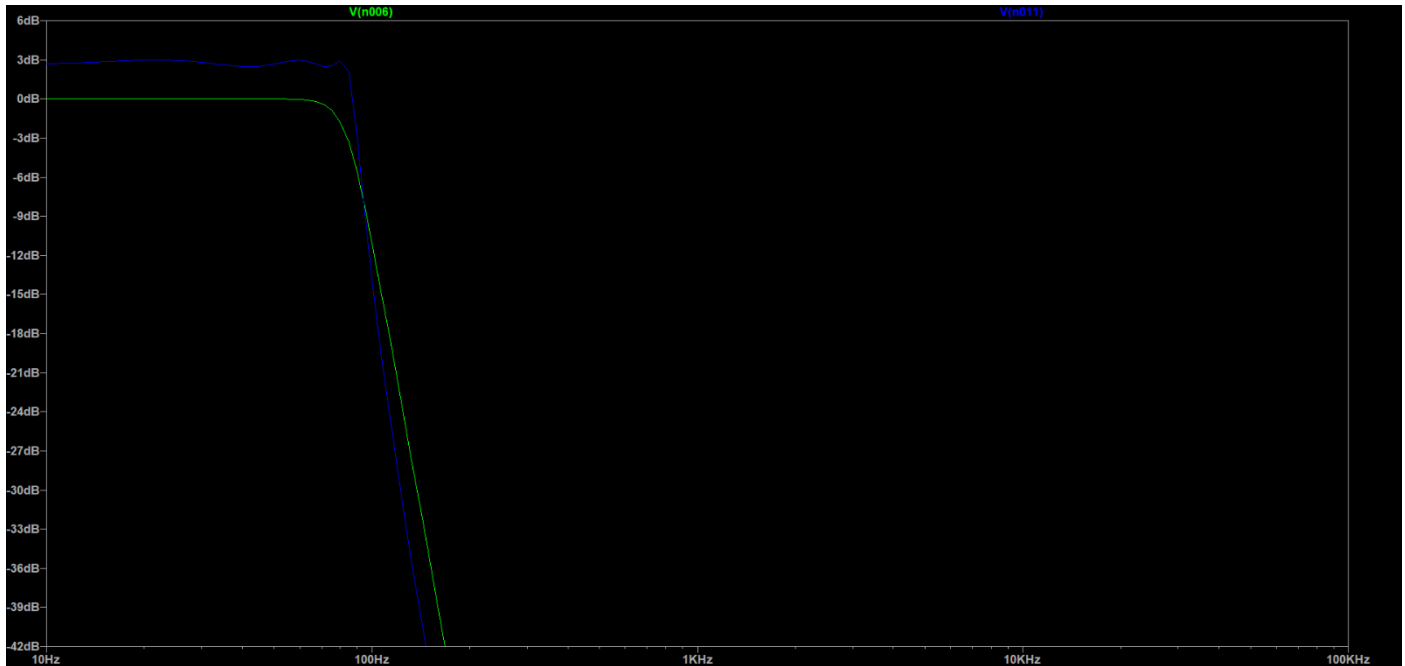

4) c.

- Butterworth (Green curve) filter in has flat passband with no ripple visible. The response is maximally flat at passband. The transition region has a broader frequency range (not a steep roll - off).
- The Chebyshev type (Blue curve) I filter has noticeable ripples in passband and it's transition region is not broader as butterworth (steeper roll-off).

5) In the case of a Butterworth filter, an order of $n=7$ is required, while the same design specifications can be met Chebyshev filter of order $n=6$. This reduction in order minimizing circuit size and complexity as well as reducing overall cost.

Additionally, the Butterworth filter exhibits a relatively wide transition band. The Chebyshev filter, on the other hand, achieves a comparatively narrower transition band, improving performance in audio. (Steeper roll-off)

Hence, **the Chebyshev filter is more suitable option** for this design.